


Combinational Logic with MSI and MSI

1. Implement the following function $F = \Sigma(0, 3, 5, 6, 7)$
 (2021) a) Decoder. b) Multiplexer c) P47.

Solution:

$$F(A, B, C) = \Sigma(0, 3, 5, 6, 7)$$

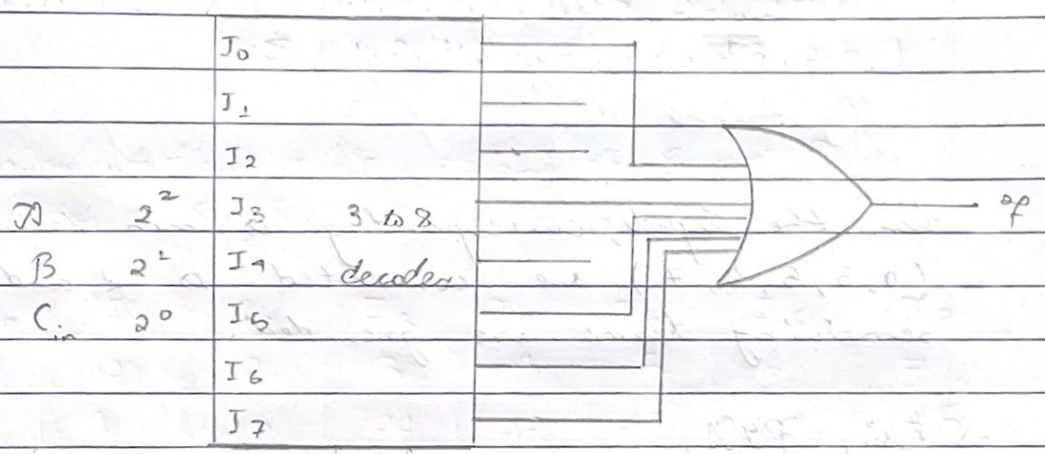a) Here, the function has 3 inputs (A, B, C) and 8 outputs. So, we'll use 3:8 decoder to implement this function.



b) Using multiplexer:

Let $F(A, B, C) = \Sigma(0, 3, 5, 6, 7)$

here, it has to be 3 inputs and 8x1 MUX should be implemented.

Let S₀, S₁, S₂ be three status lines.

Implementation table:

	I ₀	I ₁	I ₂	I ₃	I ₄	I ₅	I ₆	I ₇
A'	0	1	2	3	4	5	6	7
A	8	9						
	1	0	0	1	0	0	1	1

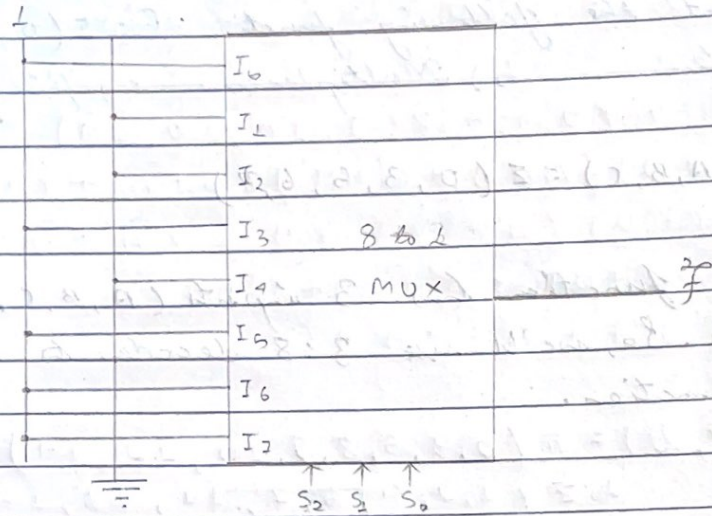


Fig. Block Diagram of 8 to 1 Multiplexer

Here, the inputs, corresponding to min terms, (0, 3, 5, 6, 7) are connected to 1 and the remaining terms are grounded.

c) Using PYN,

$$F = \Sigma(0, 3, 5, 6, 7)$$

K map for given function:

A \ BC	00	01	11	10
0	1	0	1	0
1	0	1	1	1

~~$$F_{\text{real}} = x'y'z' + xz$$~~

$$F_{\text{real}} = A'B'C' + AC + AB + BC$$

$$\text{Compliment} = AB'C' + A'B'C + A'BC'$$

here, No. of input buffers = no. of variable
= 3 (i.e. A, B, C)

No. of programmable AND gate
= No. of min terms
= 4.

No. of programmable OR gate:
= No. of output functions.
= 1.

