



Solution:

$$f = \Sigma (1, 2, 3, 4, 8)$$

a) Decoder

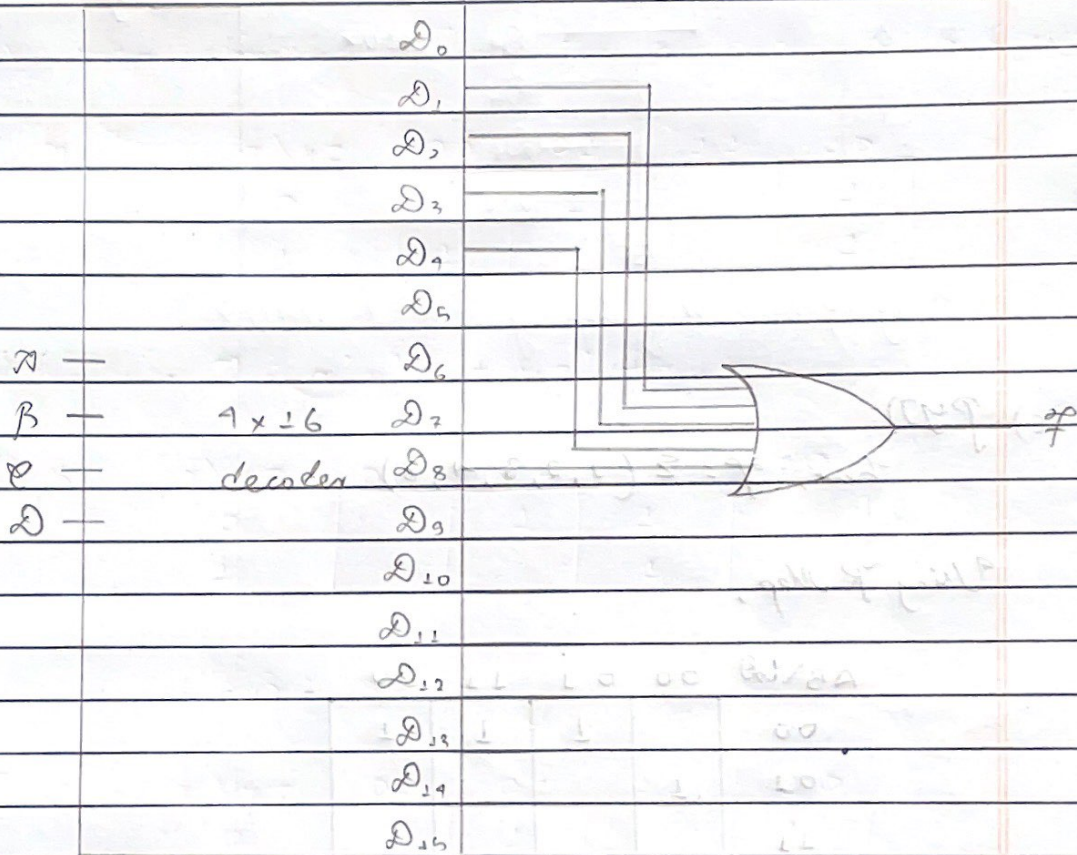


Fig Implementation of f using 4×16 Decoder

b) Multiplexer:

Let A be the input lines and B, C & D be selection lines.

Implementing with 8:1 MUX, we get,

	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
A'	0	(1)	(2)	(3)	(4)	5	6	7
A	(8)	9	10	11	12	13	14	15
A	A'	A'	A'	A'	A'	0	0	0

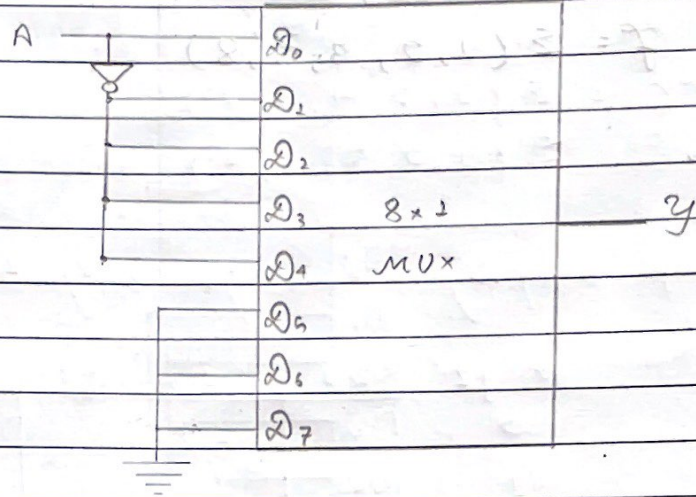
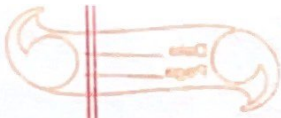


Fig Block diagram of 8:1 MUX

c) PYN:

$$\text{here, } \Sigma f = \Sigma (1, 2, 3, 4, 8)$$

Using K Map,

AB \ CD	00	01	11	10
00		1	1	1
01	1			
11				
10	1			

$$\therefore \Sigma f = A'B'C + A'B'ED + A'BC'D' + AB'C'D'$$

her,

No. of input buffers = 3 (ie. A, B, C, D)

No. of programmable AND gate

= No. of min-terms = 4

No. of programmable OR gate

= No. of output functions = 1

