

8. Implement half adder using 2-4 decoder.
ans:- Solution:

Truth table of half adder:

Input		Output	
x	y	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Truth table of decoder:


Input		Output			
x	y	D ₀	D ₁	D ₂	D ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

Comparing the above truth tables, we get,

$$\text{Sum} = D_1 + D_2$$

$$\text{Carry} = D_3$$

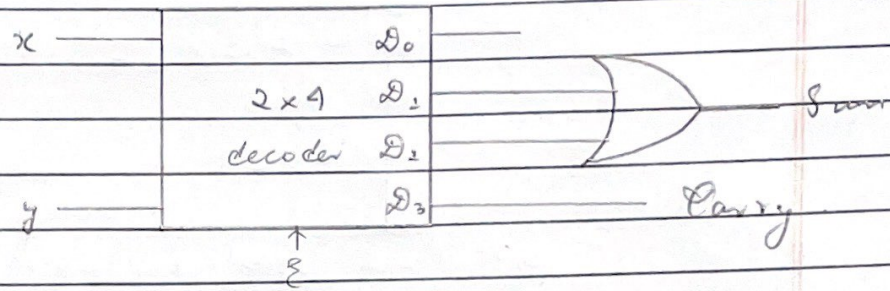Block diagram of Half adder using 2-4 decoder:



Note:

By connecting an OR gate with output Pin 1 and 2 of 2x4 decoder, half adder can be implemented.

Similarly, by connecting two half adders, we can form a Full Adder by using two, 2x4 Decoder IC's.